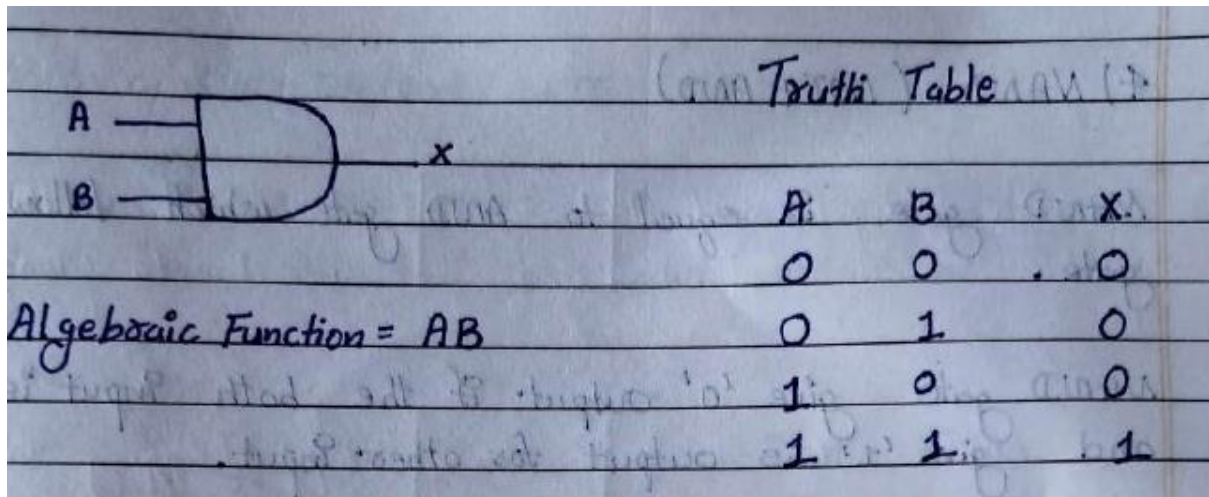


ALU Arithmetic & Logic Unit


CU Control Unit

Logic Gates


AND (.)




OR(+)

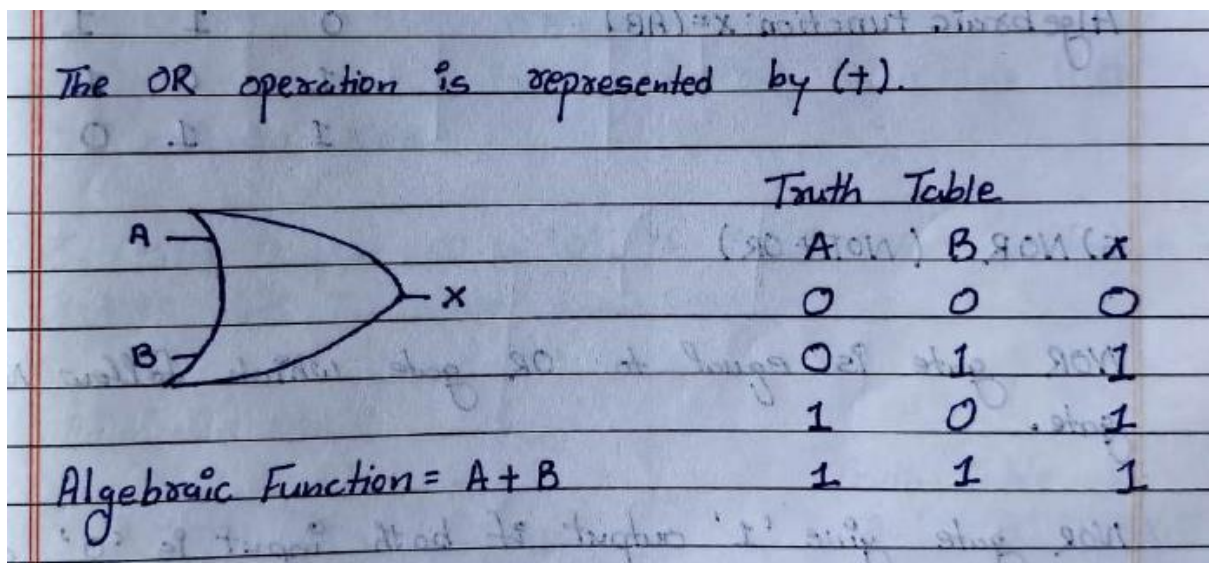

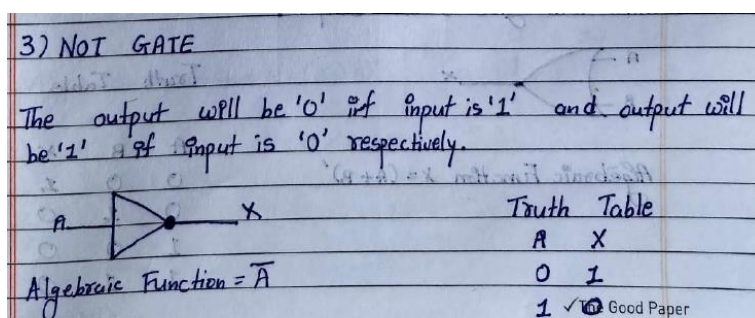
NOT( $0 \rightarrow 1, 1 \rightarrow 0$ )




NAND(NOT+AND)

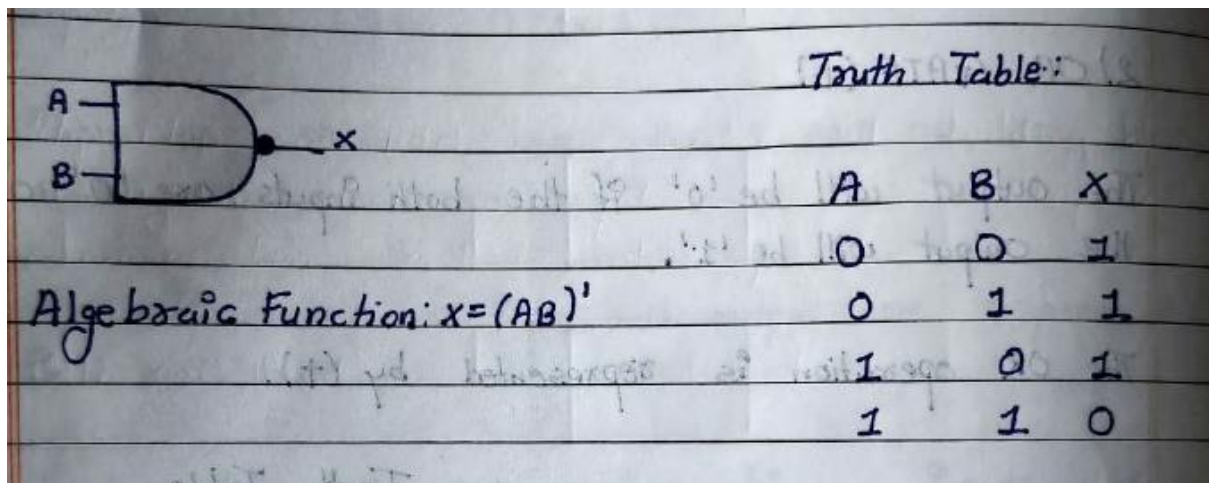


NOR(NOT+OR)

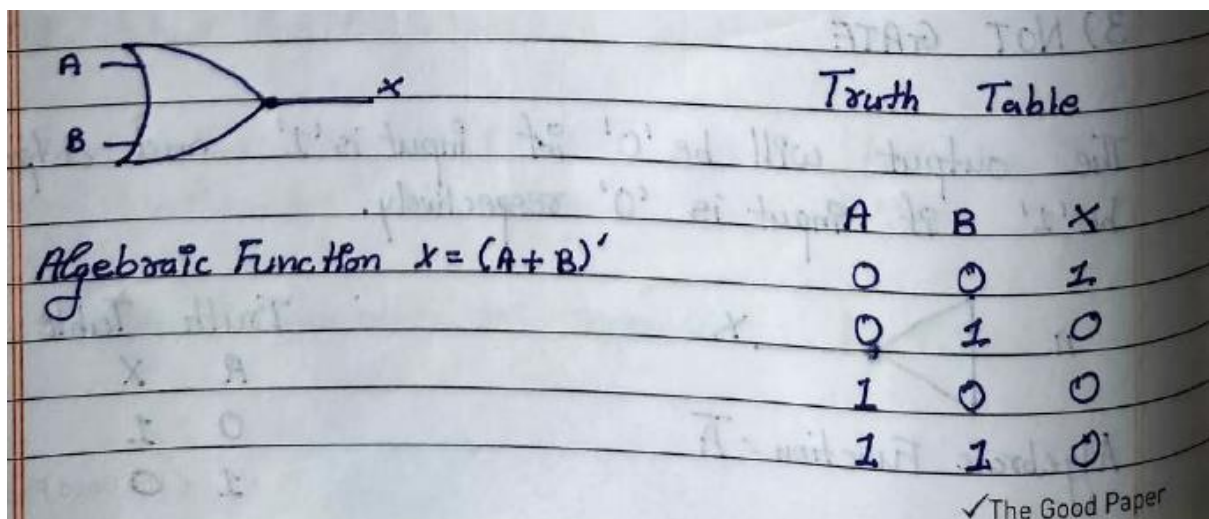

Exclusive OR(or XOR)

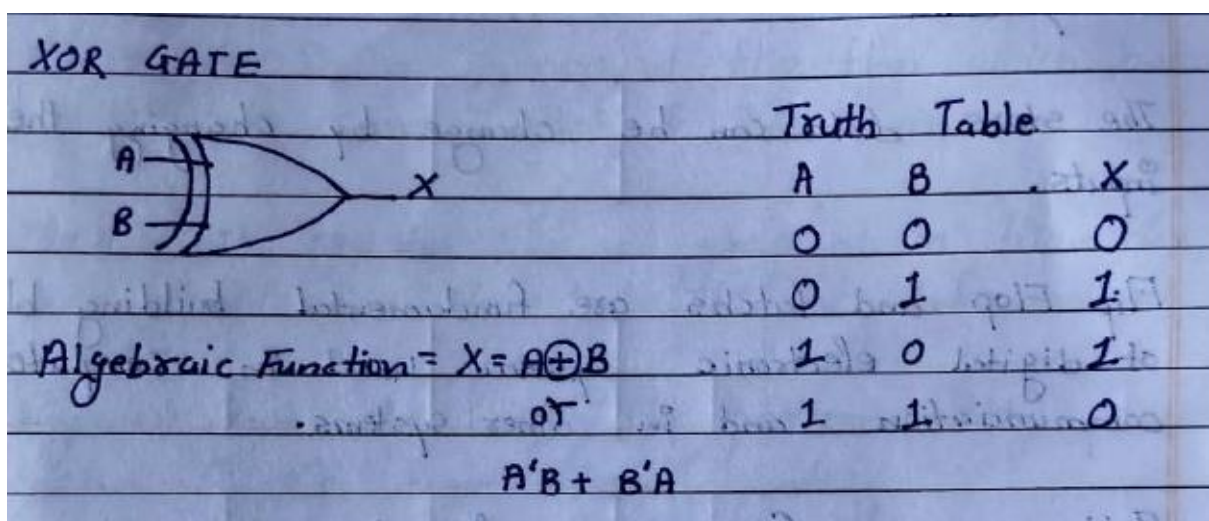

## Exclusive NOR

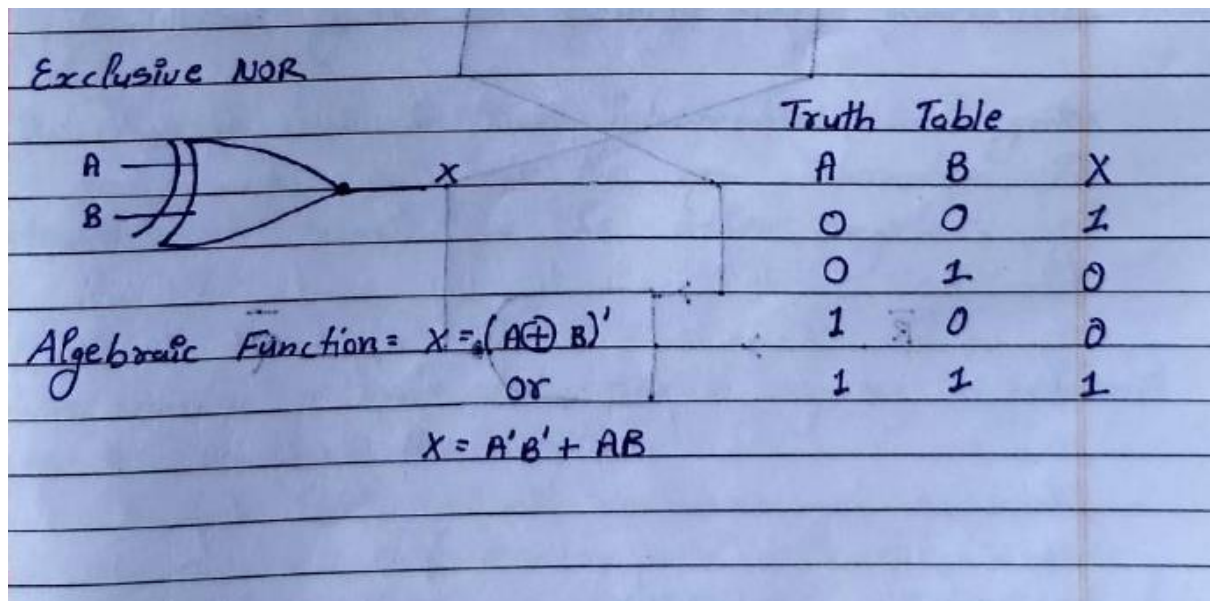

Micro-operation (Operation that can be performed on the data stored in register.)

Types of Micro-operation:


Arithmetic

Logic

Shift

Multiplexer:  $2^n$  inputs has "N" selective lines.

It's also known as MUX.

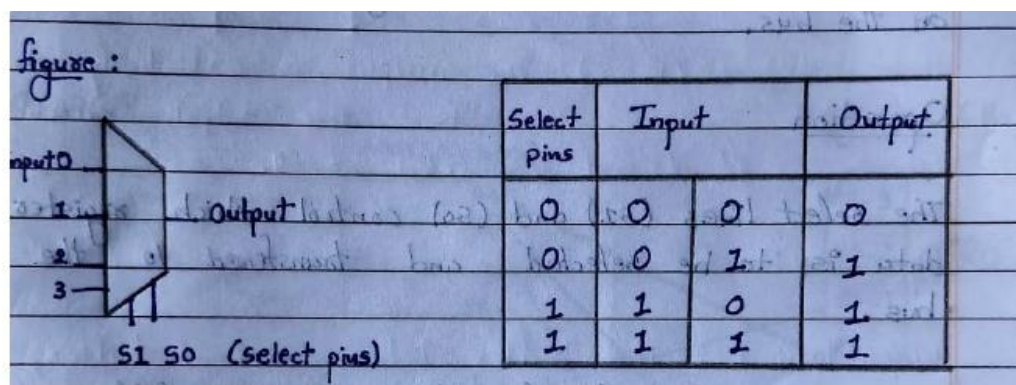



## Tri state buffer

A tri-state buffer is a type of digital electronic component that can exist in one of three states: high (1), low (0), or high impedance (Z). The high impedance state effectively disconnects the buffer from the circuit, allowing multiple outputs to be connected to a single line without interference. Here's a more detailed explanation:

### Tri-State Buffer


#### States:

1. **High (1):** The buffer outputs a high voltage level, representing a binary 1.
2. **Low (0):** The buffer outputs a low voltage level, representing a binary 0.
3. **High Impedance (Z):** The buffer is in a high impedance state, essentially disconnected from the circuit, allowing other components to drive the line.
 
#### Control Line:

A tri-state buffer has an additional control line (enable line) that determines its output state:

- **Enabled (Control Line Active):** The buffer outputs either high (1) or low (0) based on the input.
- **Disabled (Control Line Inactive):** The buffer goes into high impedance (Z) state, effectively disconnecting from the circuit.




Decoder:

The circuit which change the binary information into  $2^N$  output known as decoder.

The binary information is passed in the form of  $N$  input lines.

In simple word the decoder is reverse of Encoder.

The diagram of decoder is as follow:

 


Half Adder (XOR+AND GATES ARE USED)


$$\text{SUM} = x'y + y'x$$

$$\text{Carry} = xy$$

Diagram of half adder.

 


Full Adder (2 Half Adder+ OR gate)

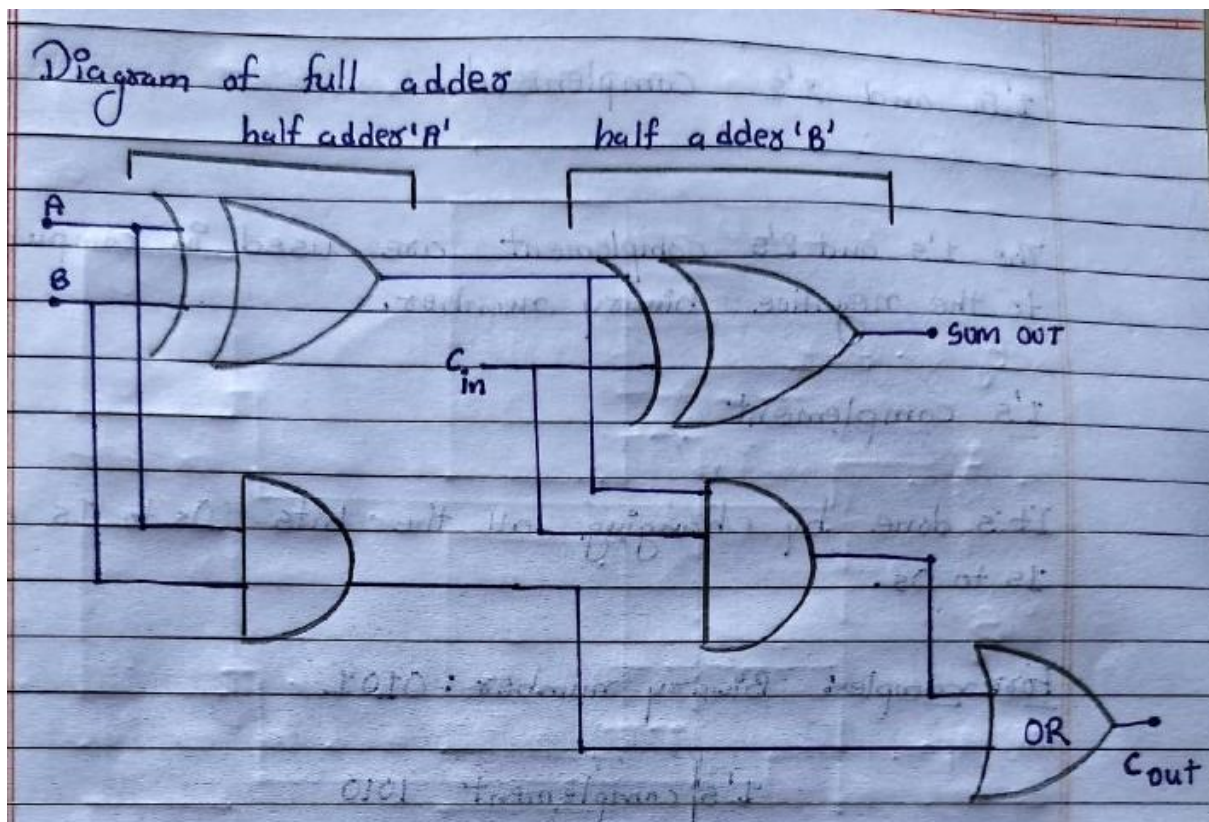

Types of Addressing of Memory
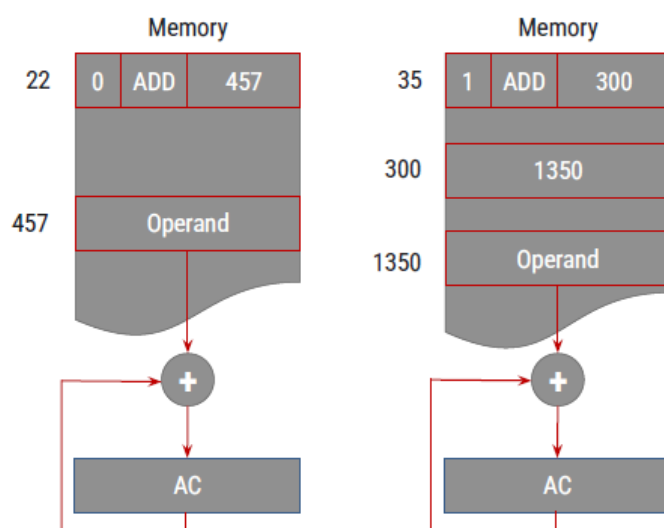
### Direct & Indirect Addressing of Memory



□ If the second part of an instruction format specifies the address of an operand, the instruction is said to have a **direct address**.

□ In **Indirect address**, the bits in the second part of the instruction designate an address of a memory word in which the address of the operand is found.

## Direct & Indirect Addressing of Memory




- A **direct address** instruction is placed at address 22 in memory.
- The I bit is 0, so the instruction is recognized as a direct address instruction.
- The opcode specifies an ADD instruction, and the address part is the binary equivalent of 457.
- The control finds the operand in memory at address 457 and adds it to the content of AC.



- The instruction in address 35 has a mode bit I = 1, recognized as an **indirect address** instruction.
- The address part is the binary equivalent of 300.
- The control goes to address 300 to find the address of the operand.
- The address of the operand in this case is 1350.
- The operand found in address 1350 is then added to the content of AC.

## Computer Registers

### Computer Registers

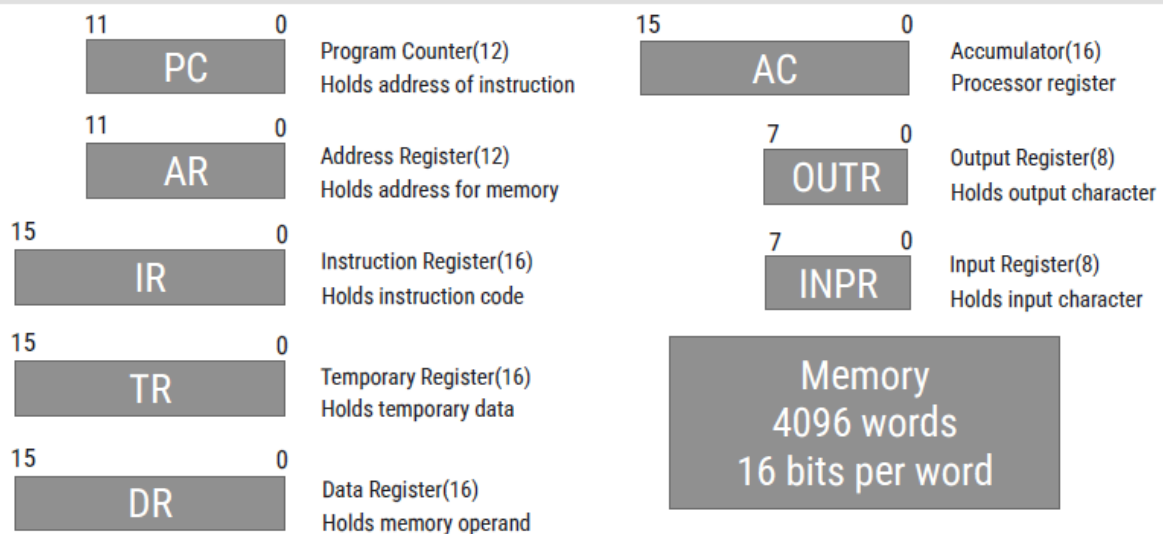

## Types of Computer Instruction:

### 1. Memory Reference Instruction

ADD : add the content of memory to AC

AND: AND the content of memory to AC

LDA: Load memory word to AC

STA: store the content of AC in memory

BUN: Branch Unconditionally

BSA: Branch and Save return address

ISZ: Increment and skip if zero

### 2. Register Reference Instruction

CLA: Clear AC

CLE: clear E

CMA: complement AC

CME: complement W

CIR: Circulate Right AC and E

CIL: Circulate left AC and E

INC: Increment AC

SPA: skip next instruction if AC is positive

SNA: skip next instruction if AC is negative

SZA: skip next instruction if AC is Zero

SZE: skip next instruction if E is zero

HLT: halt computer

### 3. Input output instruction

INP: Input character to AC

OUT: Output character to AC

SKI: Skip on input flag



SKO: skip on output flag

ION: interrupt on

IOF: interrupt off

Parts of CPU:

### **1. Arithmetic Logic Unit (ALU)**

**Definition:** Performs arithmetic and logical operations, such as addition, subtraction, AND, OR, and NOT.

### **2. Control Unit (CU)**

**Definition:** Directs the operation of the processor by fetching, decoding, and executing instructions from memory.

### **3. Registers**

**Definition:** Small, high-speed storage locations within the CPU used to temporarily hold data and instructions.

### **4. Cache Memory**

**Definition:** A small, high-speed memory located close to the CPU to reduce the time needed to access frequently used data and instructions.

### **5. Bus Interface**

**Definition:** Facilitates communication between the CPU and other components, such as memory and I/O devices.

### **6. Instruction Decoder**

**Definition:** Interprets binary instructions fetched from memory and translates them into signals that control other parts of the CPU.

### **7. Floating Point Unit (FPU)**

**Definition:** Handles complex arithmetic operations involving floating-point numbers.

### **8. Memory Management Unit (MMU)**

**Definition:** Manages memory access and translation of virtual memory addresses to physical addresses.